

# Processor Review

CS 1541






Wonsun Ahn

# Clocking Review

Stuff you learned in CS 447

# Logic components


- Do you remember what all these do?

 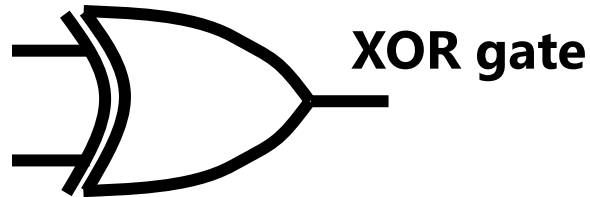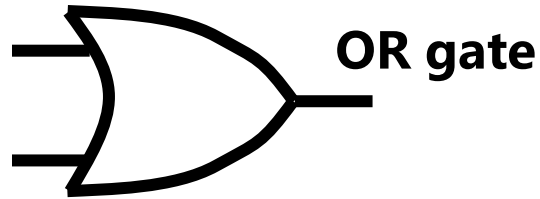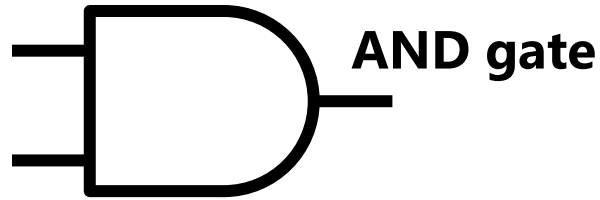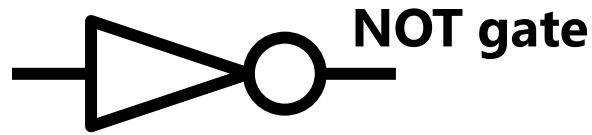

Blue wires are control signals.
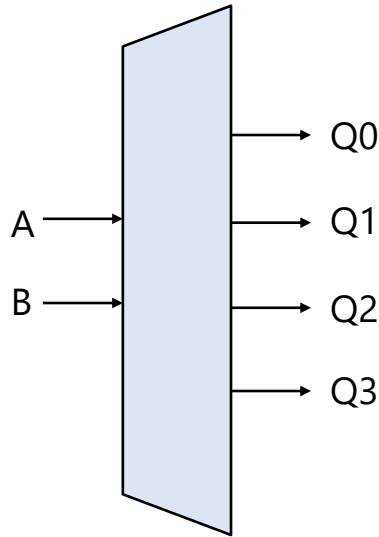
# Uses of a Decoder

- Translates a set of input signals to a bunch of output signals.
  - E.g. a binary decoder:




**Truth Table for Decoder**

A	B	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


- You can come up with any truth table and make a decoder for it!
 
# Uses of a Multiplexer

- No problem in fanning out one signal to two points




 - Cannot connect two signals to one point
  - Must use a multiplexer to *select* between the two




# Gates are made of transistors (of course)

- NOT gate

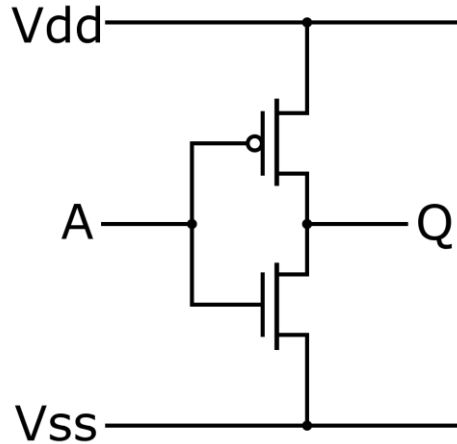


- NAND gate

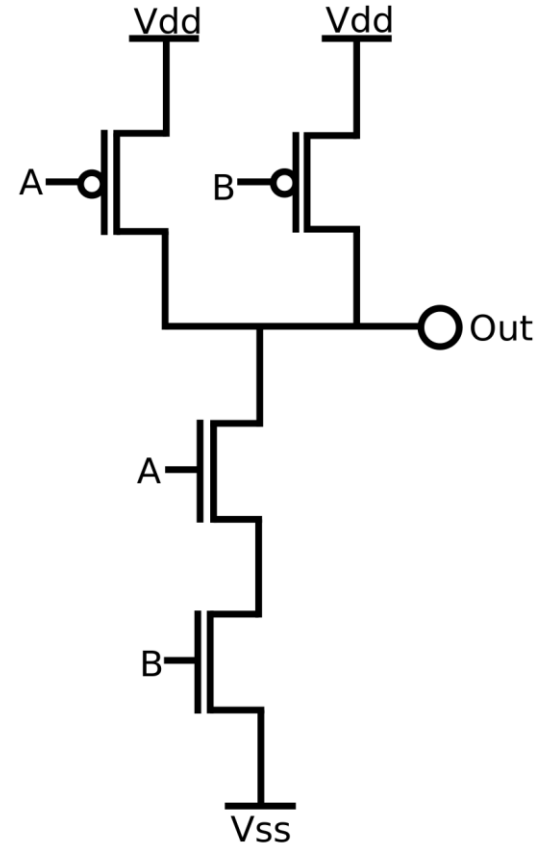
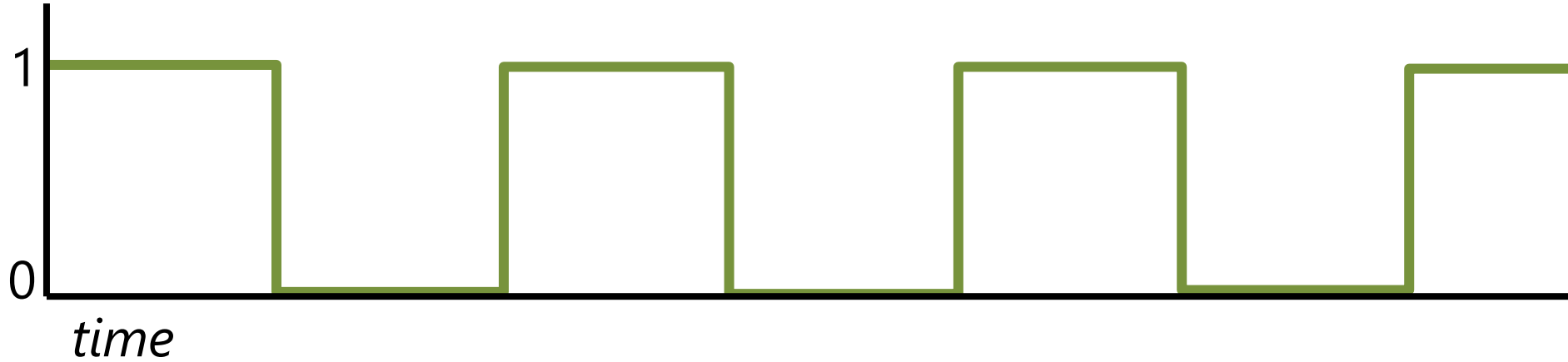
# The clock signal


- The clock is a signal that alternates regularly between 0 and 1:



- Bits are latched on to registers and flip-flops on rising edges
- In between rising edges, bits propagate through the logic circuit
  - Composed of ALUs, muxes, decoders, etc.
  - **Propagation delay**: amount of time it takes from input to output
 
# Critical Path

- **Critical path**: path in a circuit that has longest propagation delay
  - Determines the overall clock speed.



- The ALU and the multiplexer both have a 5 ns delay
- How fast can we clock this circuit?
  - Is it  $1 / 5 \text{ ns}$  ( $5 \times 10^{-9} \text{ s}$ ) = 200 MHz?
  - Or is it  $1 / 10 \text{ ns}$  ( $10 \times 10^{-9} \text{ s}$ ) = 100 MHz? ✓



# MIPS Review

Stuff you learned in CS 447

# The MIPS ISA - Registers

- MIPS has 32 32-bit registers, with the following usage conventions
  - But really, all are general purpose registers (nothing special about them)

Name	Register number	Usage
<b>\$zero</b>	<b>0</b>	the constant value 0 (can't be written)
<b>\$at</b>	<b>1</b>	assembler temporary
<b>\$v0-\$v1</b>	<b>2-3</b>	values for results and expression evaluation
<b>\$a0-\$a3</b>	<b>4-7</b>	function arguments
<b>\$t0-\$t7</b>	<b>8-15</b>	unsaved temporaries
<b>\$s0-\$s7</b>	<b>16-23</b>	saved temporaries (like program variables)
<b>\$t8-\$t9</b>	<b>24-25</b>	more unsaved temporaries
<b>\$k0-\$k1</b>	<b>26-27</b>	reserved for OS kernel
<b>\$gp</b>	<b>28</b>	global pointer
<b>\$sp</b>	<b>29</b>	stack pointer
<b>\$fp</b>	<b>30</b>	frame pointer
<b>\$ra</b>	<b>31</b>	return address

# The MIPS ISA - Memory

- MIPS is a **RISC (reduced instruction set computer)** architecture
- It is also a **load-store** architecture
  - **All** memory accesses performed by load and store instructions
- Memory is a giant array of  $2^{32}$  bytes

Addr	Data
0	0x3F
1	0x00
2	0x2A
3	0x08
4	0x47
5	0xF4
6	0x26
7	0xB9
...	...

Addr	Data
0	0x3F00
2	0x2A08
4	0x47F4
6	0x26B9
...	...

Addr	Data
0	0x3F002A08
4	0x47F426B9
...	...

- The same memory viewed as bytes, 16-bit halfwords, and 32-bit words (using big-endian)
- All addresses are **aligned** (multiples of data size)

# The MIPS ISA - Memory

- Loads move data *from* memory *into* the registers.

**lw** **\$t0**, **8(\$s4)**

This is the address, and it means "the value of \$s4 + 8."

t0	0x0000BEEF
s4	0x00000004

**Registers**

- Stores move data *from* the registers *into* memory.

**sw** **\$t0**, **12(\$s4)**

\$t0 is the SOURCE!

lw

sw

$\$s4 + 8$


$\$s4 + 12$

0	0x3F002A08
4	0x47F426B9
8	0x00000000
12	0x0000BEEF
16	0x0000BEEF
...	...

**Memory**
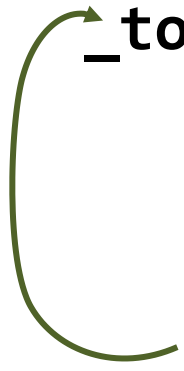
# The MIPS ISA – Flow control


- Jump and branch instructions change the flow of execution.



```
_top:
# ....
# Lots o' code
# ....
j _top
```

**j** : jumps *unconditionally*

- jumps to **\_top**

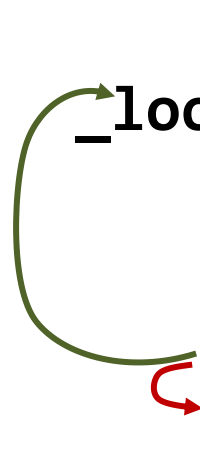

```
li    $s0, 10
_loop:
# ....
addi  $s0, $s0, -1
bne   $s0, $zero, _loop
jr    $ra
```

**bne** : jumps *conditionally*


If **\$s0** != **\$zero**, jumps to **\_loop**

If **\$s0** == **\$zero**, continues to **jr \$ra**

# Phases of instruction execution

- In most architectures, there are five phases:
  1. **IF** (Instruction Fetch) – get next instruction from memory
  2. **ID** (Instruction Decode) – figure out what instruction it is
  3. **EX** (Execute – ALU) – do any arithmetic
  4. **MEM** (Memory) – read or write data from/to memory
  5. **WB** (Register Writeback) – write any results to the registers
- Sometimes these phases are chopped into smaller stages

# A simple single-cycle implementation

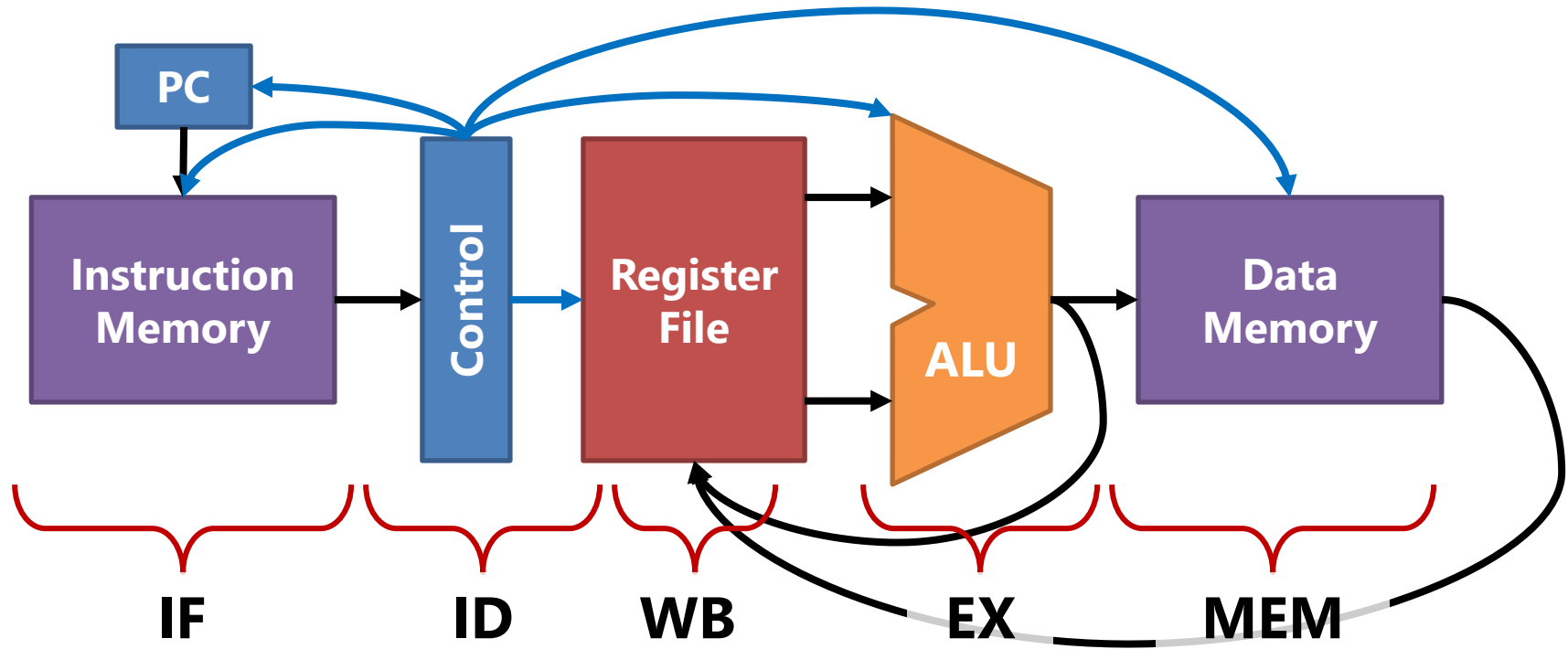

- An instruction goes through IF/ID/EX/MEM/WB in one cycle

# "Minimal MIPS"

---




# It's a "subset" of MIPS

- For pedagogical (teaching) purposes
- Contains only a minimal number of instructions:
  - **lw, sw, add, sub, and, or, slt, beq, and j**
  - Other instructions in MIPS are variations on these anyway
- Let's review the Minimal MIPS CPU focusing on the control signals
  - Again, these control signals are decoded from the instruction
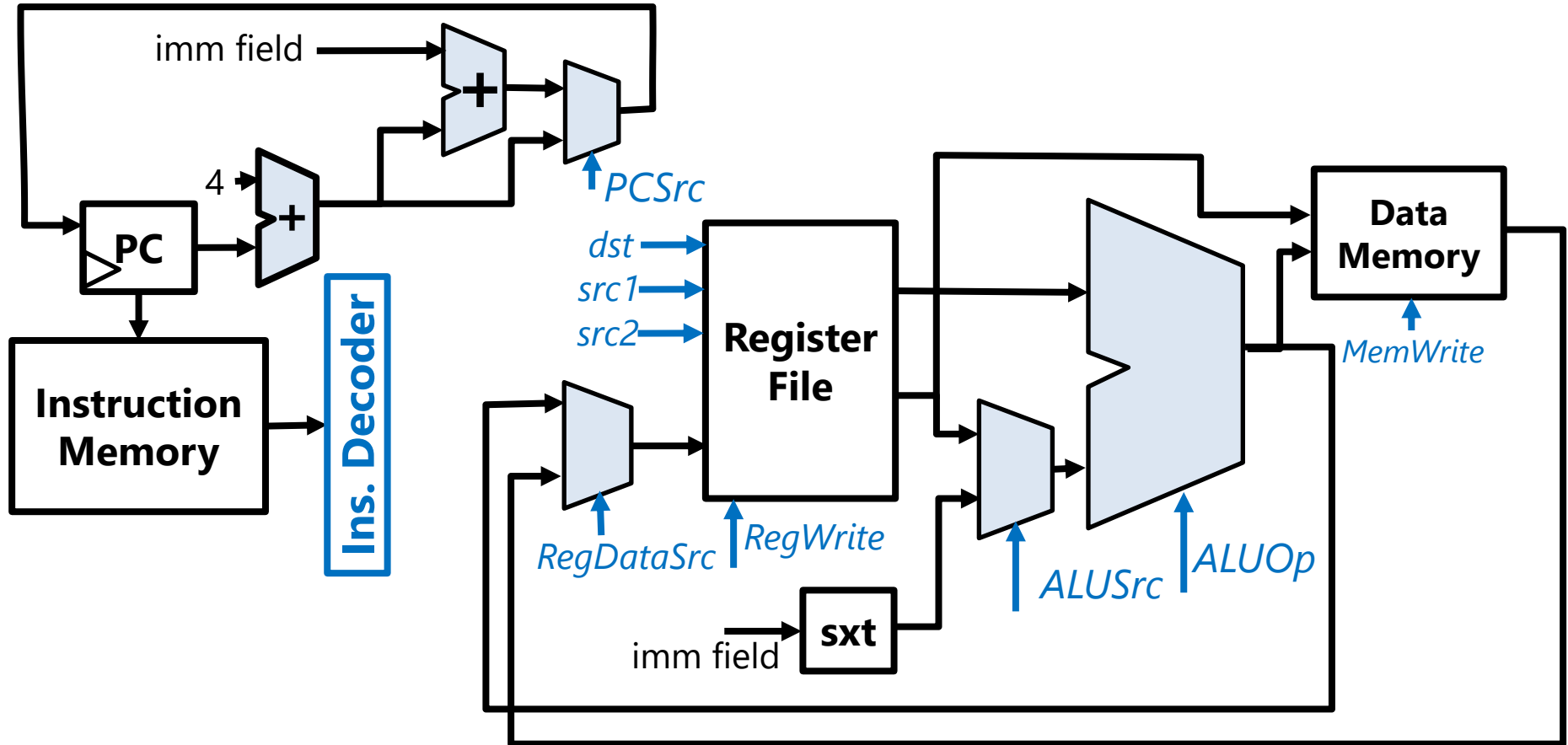
# The Minimal MIPS single-cycle CPU

- A more detailed view of the 5-phase implementation




# Control signals


- Registers
  - **RegDataSrc**: controls source of a register write (ALU / memory)
  - **RegWrite**: enables a write to the register file
  - **src1, src2, dst**: the register number for each respective operand
- ALU
  - **ALUSrc**: whether second operand of ALU is a register / immediate
  - **ALUOp**: controls what the ALU will do (add, sub, and, or etc)
- Memory
  - **MemWrite**: enables a write to data memory
- PC
  - **PCSrc**: controls source of next PC ( $PC + 4$  /  $PC + 4 + imm$ )

→ All these signals are decoded from the instruction!


# How an **add/sub/and/or/slt** work

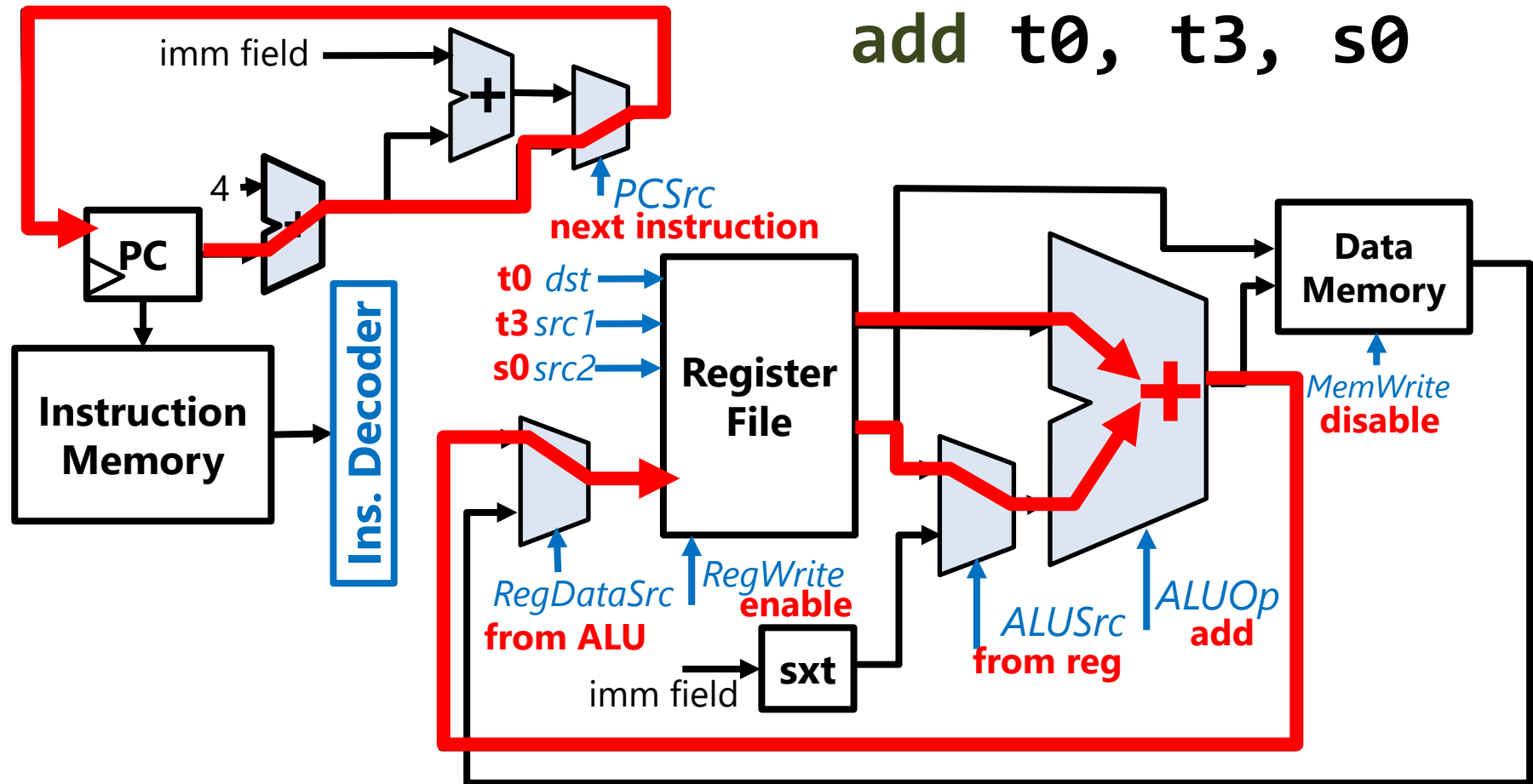

# How an **lw** works

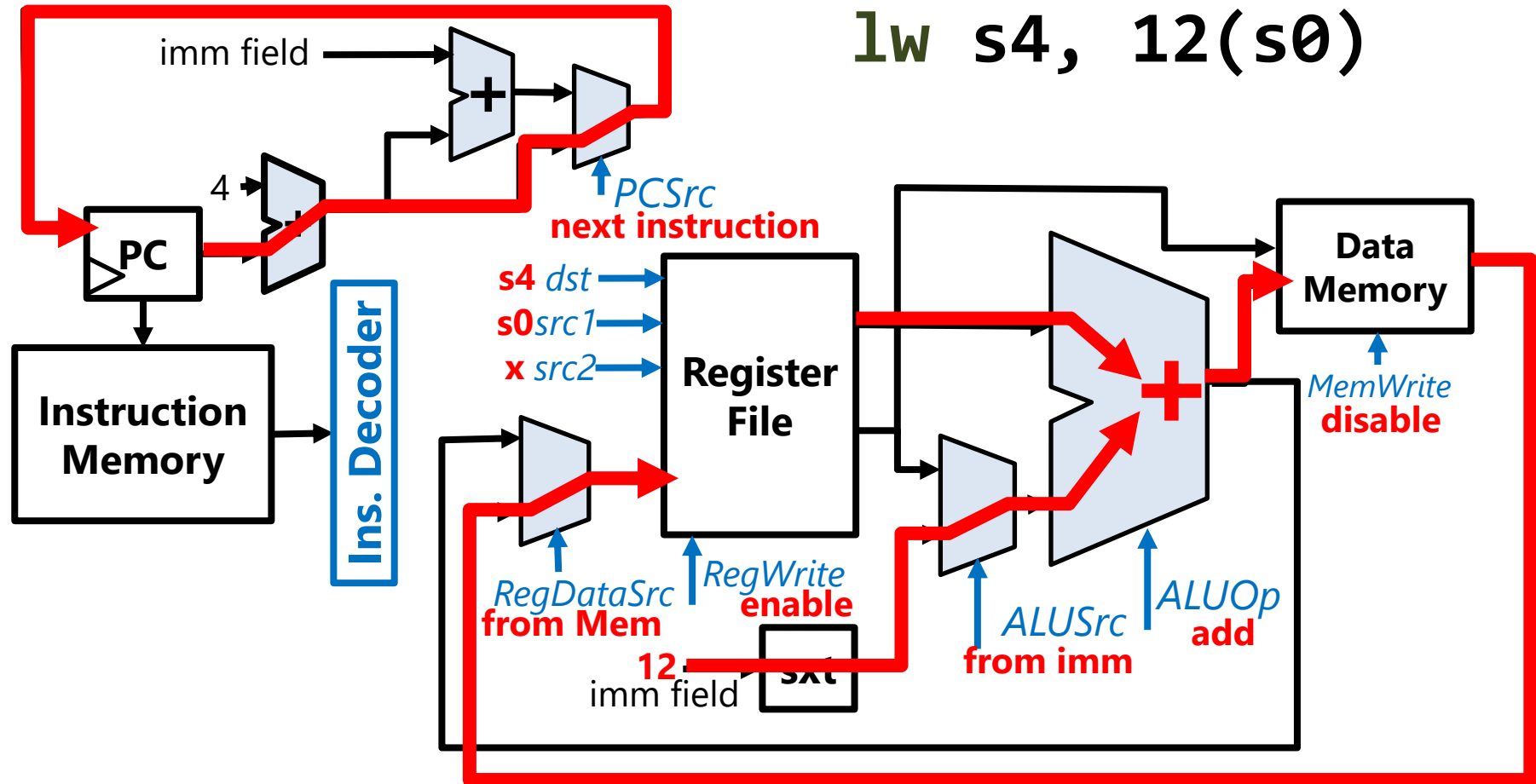


# How an **sw** works

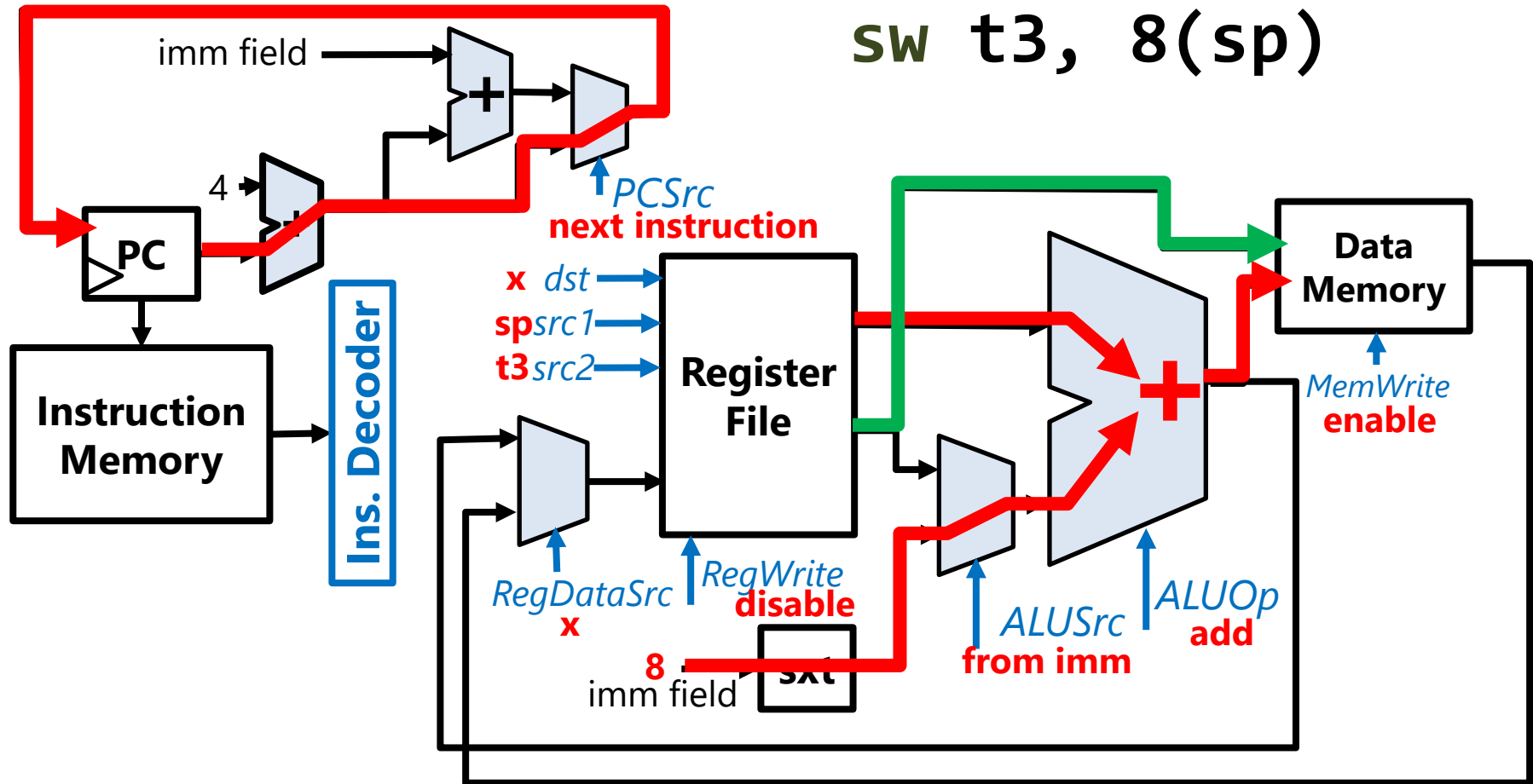
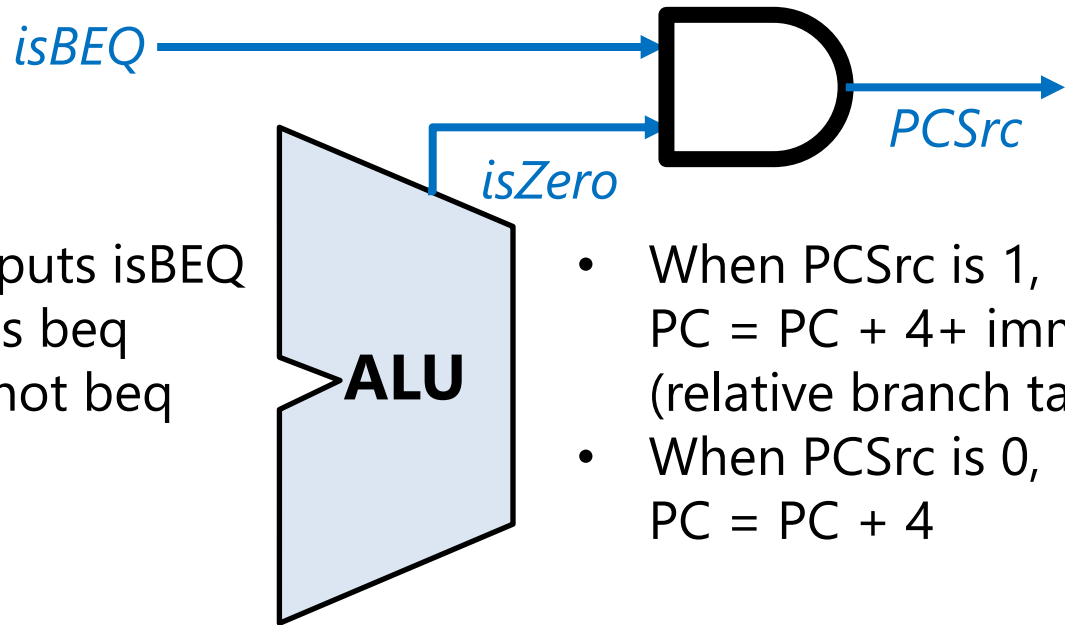
# What about **beq**?

- Compares numbers by subtracting and see if result is 0
  - If result is 0, we set PCSrc to use the branch target.
  - Otherwise, we set PCSrc to  $PC + 4$ .



- Instruction decoder outputs *isBEQ*
  - 1: When instruction is **beq**
  - 0: When instruction not **beq**


- When *PCSrc* is 1,  
 $PC = PC + 4 + \text{imm}$   
(relative branch target)
- When *PCSrc* is 0,  
 $PC = PC + 4$

# How a **beq** works

**beq t0, t1, loop**

Take green PC path when  $t0 == t1$

Take red PC path when  $t0 \neq t1$

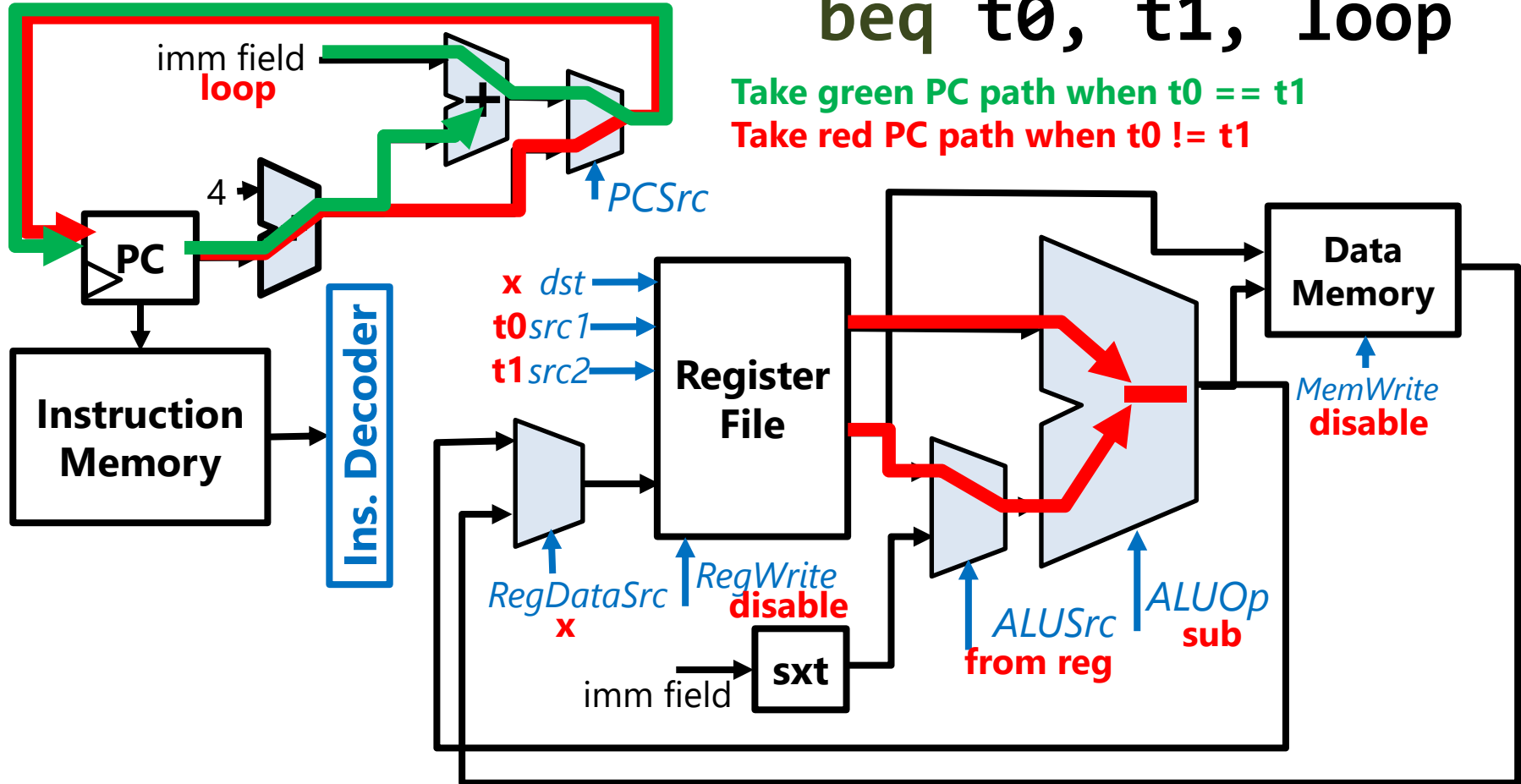





# What about **j**?

- We have to add another input to the PCSrc mux.

**j**    **top**

 
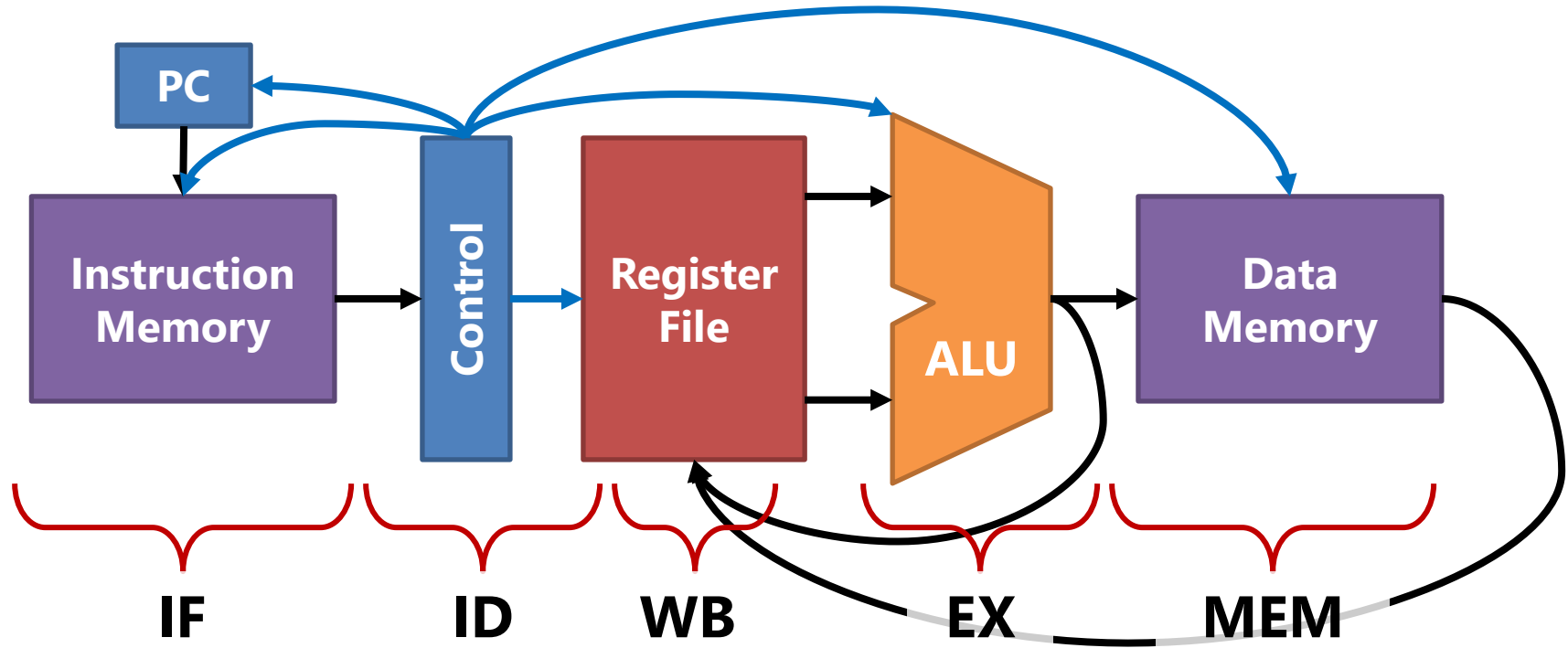
# A Single-cycle Implementation is not Optimal



- Why? Since the **longest** critical path must be chosen for cycle time
  - And there is a wide variation among different instructions

# A Single-cycle Implementation is not Optimal


- In our CPU, the **lw** instruction has the longest critical path
  - Must go through all 5 stages: IF/ID/EX/MEM/WB
  - Whereas **add** goes through just 4 stages: IF/ID/EX/WB
- If each phase takes *1 ns* each, cycle time must be *5 ns*:
  - Because it needs to be able to handle **lw**, which takes *5 ns*
  - **add** also takes *5 ns* when it could have been done in *4 ns*

Q) If **lw** is 1% and **add** is 99% of instruction mix,  
what is the average instruction execution time?

A) Still *5 ns*! Even if **lw** is only 1% of instructions!
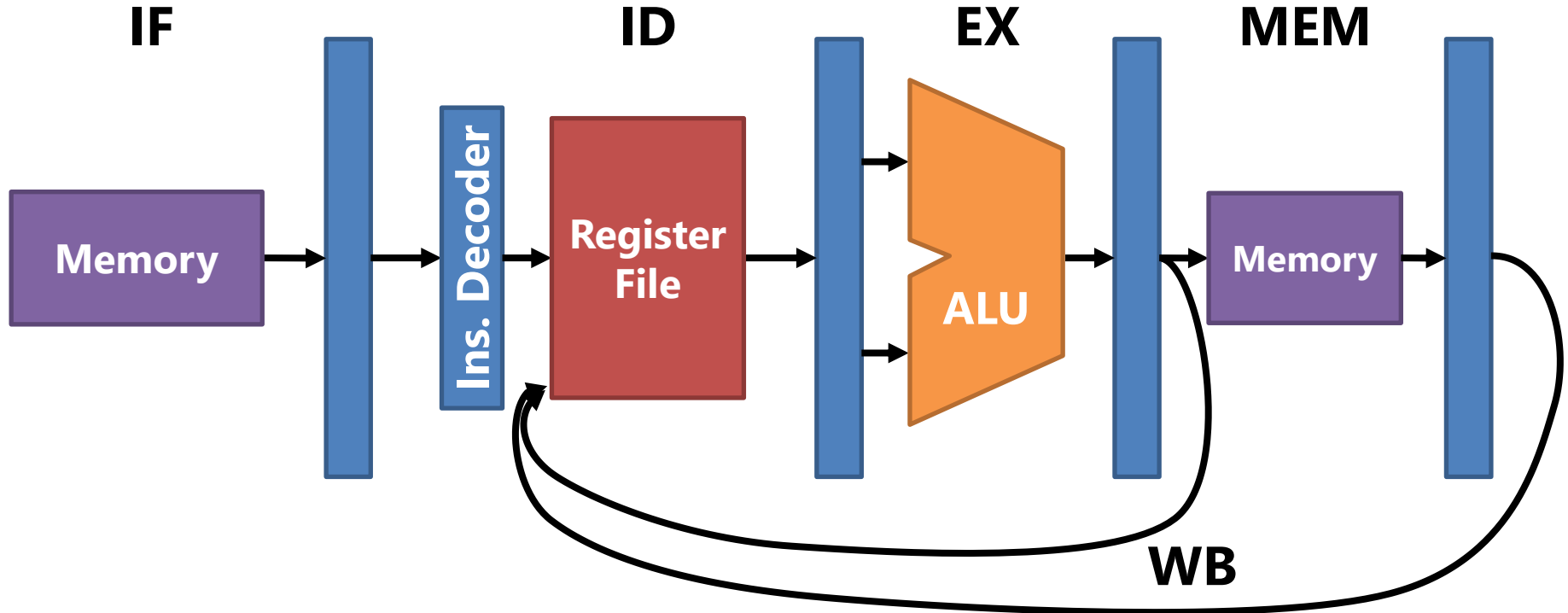
# A Multi-cycle Implementation

- It takes one cycle for each phase through the use of internal latches



# A Multi-cycle Implementation is Faster!

- Now each instruction takes different number of cycles to complete
  - **lw** takes 5 cycles: IF/ID/EX/MEM/WB
  - **add** takes 4 cycles: IF/ID/EX/WB
- If each phase takes  $1\text{ ns}$  as before:
  - **lw** takes  $5\text{ ns}$  and **add** takes  $4\text{ ns}$

Q) If **lw** is 1% and **add** is 99% of instruction mix, what is the average instruction execution time?

A)  $0.01 * 5\text{ ns} + 0.99 * 4\text{ ns} = 4.01\text{ ns}$  (25% faster than single cycle)

*\* Caveat: delay due to the added latches not shown, but net win*

# And we can do even better!

- Did you notice?
  - When an instruction is on a particular phase (e.g. IF) ...
  - ... other phases (ID/EX/MEM/WB) are not doing any work!
- Our CPU is getting chronically ***underutilized***!
  - If CPU is a factory, 80% (4/5) of the workers are idling!
- Car factories create an assembly line to solve this problem
  - No need to wait until a car is finished before starting on next one
  - Our CPU is going to use a ***pipeline*** (similar concept)